Unit 1: Slide Switch

Light Bulb

Turn on the switch 15, and the bulb lights up; turn off the switch 15, and the bulb goes out.

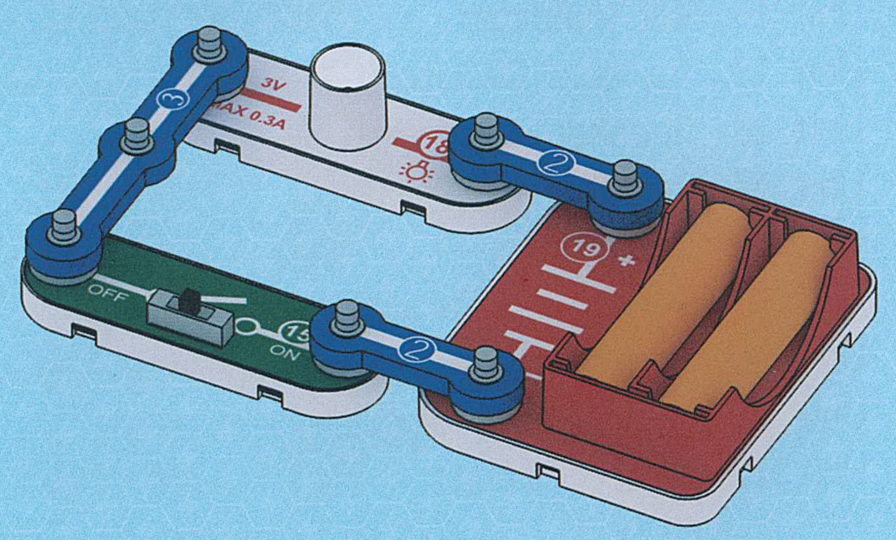

Parts Introduction

A switch is an electronic component that can open a circuit, interrupt the flow of current, or direct it to other circuits.

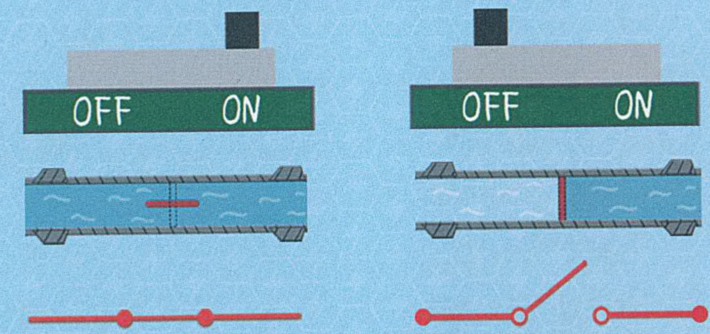

Circuit Symbol

Circuit Symbol

When the switch is set to the ON position, the circuit is completed.

When the switch is set to the OFF position, the circuit is broken.

Electric current is like water flow, and a switch is like a faucet.
When you want to break the circuit, you can close the switch (faucet);
When you want to complete the circuit, you can open the switch (faucet).

Switch Symbol

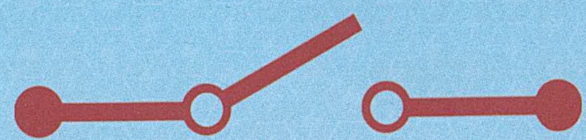

Tact Switch

rts Introduction

ct switch is a recoverable switch that can be
sed and released.

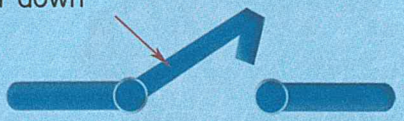

Tact Switch Symbol

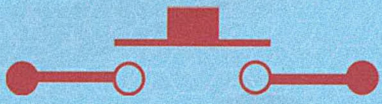

rts Introduction

ight bulb is made based on the principle of the thermal effect ectric current. When the light bulb is connected to the rated ge, the current passing through the filament heats it to an descent state (over 2000°C), causing it to emit light and heat, by

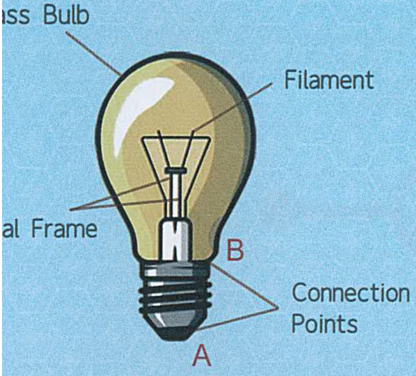

Bulb Symbol

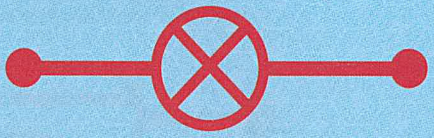

Tact Switch

rts Introduction

ct switch is a recoverable switch that can be
sed and released.

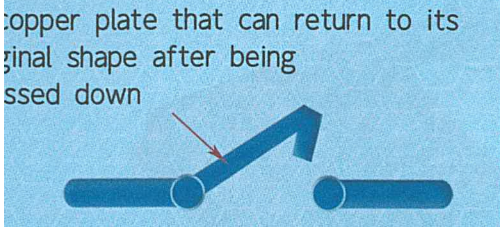

Tact Switch Symbol

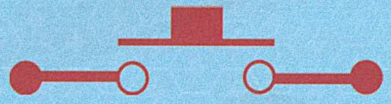

rts Introduction

ight bulb is made based on the principle of the thermal effect
ectric current. When the light bulb is connected to the rated
ge, the current passing through the filament heats it to an
descent state (over 2000°C), causing it to emit light and heat,
by

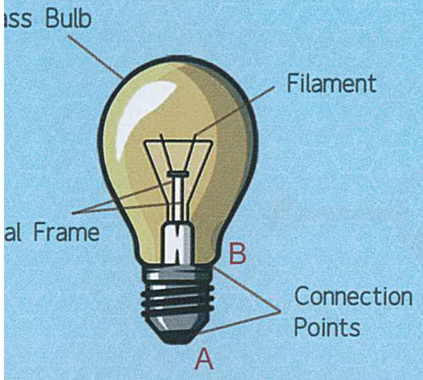

Bulb Symbol